

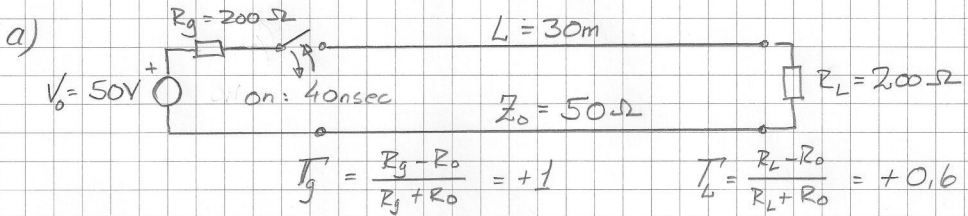
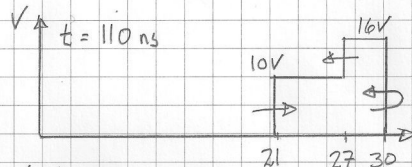


## TRANSMISSION LINES


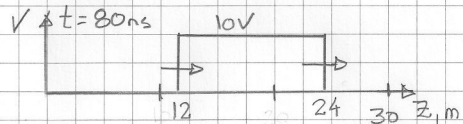


Note: Switch is opened again after 40ns, so the returning pulse will encounter an open circuit,  $R_g \rightarrow \infty$ .
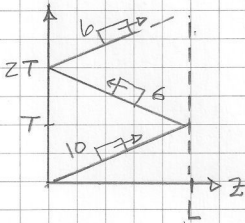
$$T = \frac{l}{c} = \frac{30}{3 \cdot 10^8} = 10^{-7} = 100 \text{ nsec}. \quad V_1 = V_0 \cdot \frac{R_0}{R_g + R_0} = 10V.$$



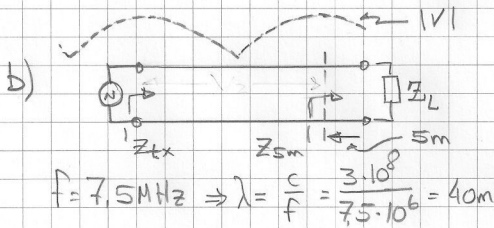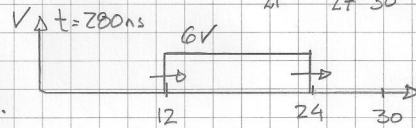At  $t = 1 \text{ minute}$  we simply have the voltage source disconnected and no voltage (0V) on the line.



$$L = \frac{30 \text{ m}}{40 \text{ m}} \lambda = 0.75 \lambda$$

$$5 \text{ m} = 5/40 \lambda = \lambda/8.$$

$$Z_{5m} = 3 \Rightarrow Z_{5m} = 3 \cdot 50 = 150 \Omega$$

$$Z_{ant} \approx 0.6 + j0.8 \rightarrow 30 + j40 \Omega$$

$$Z_{tx} \approx 0.6 - j0.8 \rightarrow 30 - j40 \Omega$$

• Draw the  $S=3$  circle on Smith chart

•  $|V|_{\text{max}}$  is on real-axis to the right.

