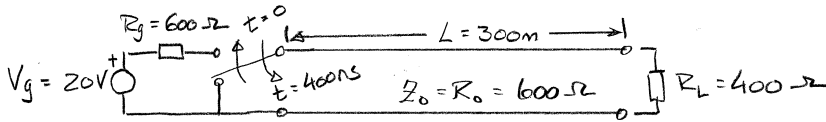


RAF 402G Exam 4-MAY-2016 PROBLEM 5.

a)




$$T = \frac{L}{c} = \frac{300}{3 \cdot 10^8} = 10^{-6} \text{ s} = 1 \mu\text{s} = 1000 \text{ ns.}$$

$$V_i = V_g \cdot \frac{R_o}{R_o + R_g} = 20 \cdot \frac{600}{1200} = 10 \text{ V}$$


$$T_L = \frac{R_L - R_o}{R_L + R_o} = \frac{400 - 600}{400 + 600} = -0,2. \quad T_g = \frac{R_g - R_o}{R_g + R_o} = \frac{0 - 600}{0 + 600} = -1$$

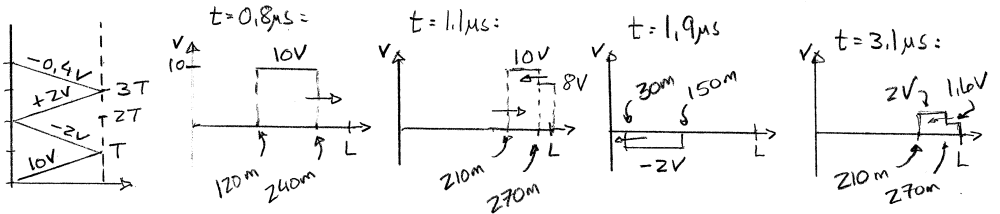After 400ns, when the pulse returns, the generator side is short circuited, so  $R_g = 0$ .



After 1 minute the line has been short circuited and the voltage is zero (0V) everywhere along the line.

b)

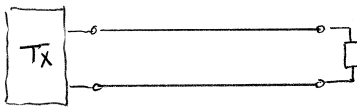

$$Z_L = 240 + j480 \Omega \quad \lambda = \frac{c}{f} = \frac{3 \cdot 10^8}{1 \cdot 10^6} = 300 \text{ m}$$

$$z_L = \frac{Z_L}{R_o} = \frac{240 + j480}{600} = 0,4 + j0,8$$

$Y_L$  is the opposite point on the Smith chart:  $Y_L = 0,5 - j1$

$$\Rightarrow Y_L = \frac{Y_L}{R_o} = \frac{0,5 - j1}{600} = 0,833 - j1,667 \text{ mS}$$

Standing wave ratio from the Smith chart:  $S = r_m = 4,4$

$$\frac{|V_{\text{max}}|}{|V_{\text{min}}|} = S \Rightarrow |V_{\text{max}}| = 10 \cdot 4,4 = 44 \text{ V}$$

