
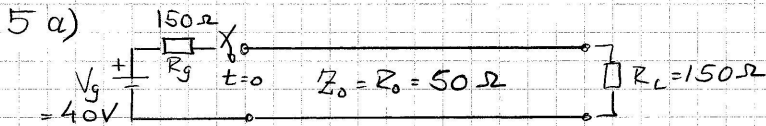
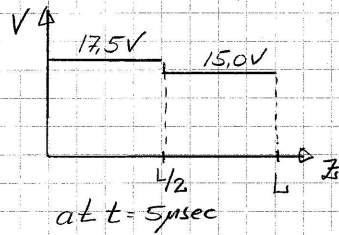


SOLUTIONS FOR EXAM 7-MAY-2013 - TRANSMISSION LINES - FINAL


$$T = \frac{L}{c} = \frac{600}{3 \cdot 10^8} = 2 \cdot 10^{-6} \text{ s} = 2 \mu\text{sec.}$$

$$\Gamma_g = \frac{R_g - R_0}{R_g + R_0} = \frac{150 - 50}{150 + 50} = +0,5 \quad \Gamma_L = \frac{R_L - R_0}{R_L + R_0} = \frac{150 - 50}{150 + 50} = +0,5$$
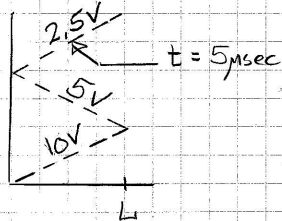
$$V_1^+ = V_g \frac{R_0}{R_g + R_0} = 40 \cdot \frac{50}{150 + 50} = 10 \text{ V.}$$



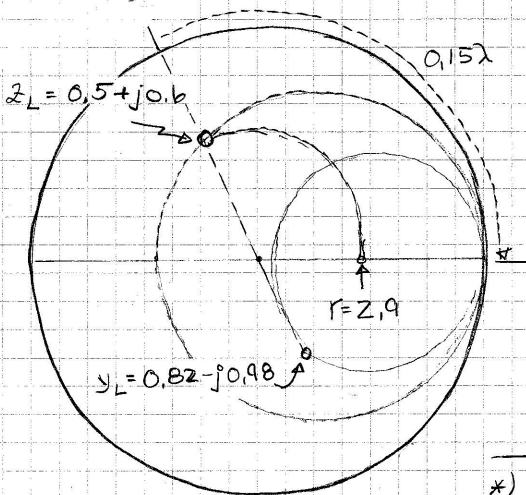5 b) $Z_L = 2,5 + j30 \Omega \Rightarrow z_L = \frac{1}{R_0} \cdot Z_L = 0,5 + j0,6$.



$$Y_L = \frac{1}{Z_L} = 16,4 - j19,6 \text{ mS}$$

$$d = 0,15 \lambda$$

$$R^* = R_0 \cdot r = 145 \Omega$$

*) The test incorrectly labelled this resistance as G , but it should read R . This was corrected during the exam.